

# Certificate

Name : Nandini Sen

Class : BSc Part II


Roll No. :


Exam No. :

Institution SH. PRAGYA MAHAVIDYALAYA BIJAINAGAR

This is certified to be the bonafide work of the student in the  
Physics Laboratory during the academic  
year 2023/2024.

No of practicals certified 10 out of 10 in the  
subject of Physics

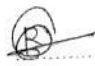  
Examiner's signature




  
Teacher in charge  
Director  
Shri Pragya Mahavidyalaya  
Bijainagar-305624  
Principal


Date : 10. Jan. 24

Institution Rubber Stamp

  
Director  
Shri Pragya Mahavidyalaya  
Bijainagar-305624

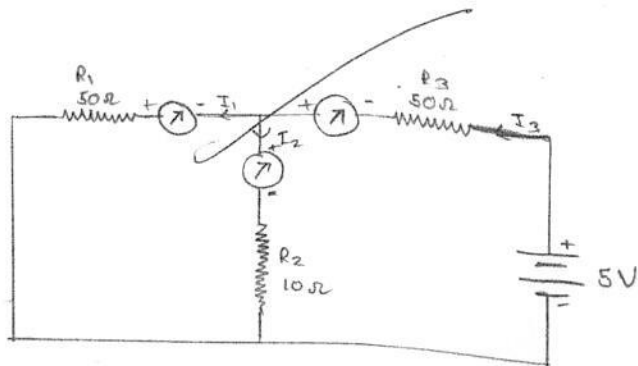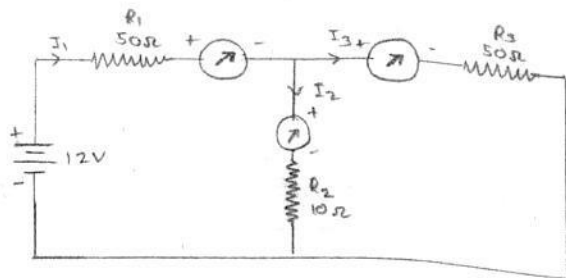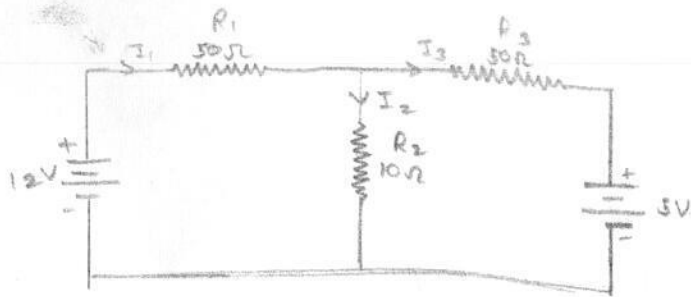(N. B : The candidate is expected to retain his/her journal till he/she passes in the subject)



  
 Director  
 Shri Pragna Mahavidyalaya  
 Bijnagar-305624

Date .....

Expt. No. .... I .....

Page No. .... 1 .....

### Experiment :- 1 Superposition Theorem

Object :- Verification of Superposition Theorem.

Equipments required :- voltmeter, ammeter, wire, circuit box.

Theory :- This theorem states that in a network of linear resistances containing more than one source of emf the current which flows at any point is the sum of all the currents which would flow at that point if each emf source (voltage source) were considered separately and all the other emf source replaced for the time being by resistance equal to their internal resistance.

4. Observation Table :-

S.No	Source	Theoretical value	Practical value
1.	12V	$I_1 = 205.7 \text{ mA}$	200 mA
2.		$I_2 = 171.4 \text{ mA}$	160 mA
3.		$I_3 = 34.2 \text{ mA}$	40 mA
4.	5V	$I_1' = 14.3 \text{ mA}$	20 mA
5.		$I_2' = 71.4 \text{ mA}$	80 mA
6.		$I_3' = 85.7 \text{ mA}$	80 mA

Teacher's Signature : .....

Calculation :- (a) Consider only 12V source :-

$$R_T = \frac{50 \times 10}{60} + 50 = 8.33 + 50 = 58.33 \Omega$$

so, Total current  $I_T = \frac{V}{R_T} = \frac{12}{58.33} = 205.7 \text{ mA}$  [∵  $R_1 \parallel R_2$ ]

$$I_1 = 205.7 \text{ mA}$$

$$I_3 = 205.7 \times \frac{10}{60} = 34.2 \text{ mA}$$

$$I_2 = I_1 - I_3 = 171.4 \text{ mA}$$

b) Consider only 5V source :-

$$R_T = 58.33 \Omega$$

Here  $I_3' = I_T$  so,  $I_T = I_3' = \frac{V}{R_T} = \frac{5}{58.33} = 85.7 \text{ mA}$

$$I_2' = \frac{85.7 \times 50}{50 + 10} = 71.4 \text{ mA}$$

$$I_1' = 85.7 - 71.4 = 14.2 \text{ mA}$$


Date .....

Expt. No. ....

Page No. 2





(6) Result :- Theoretical value and calculator calculated value is approx. same hence, superposition theorem verified.

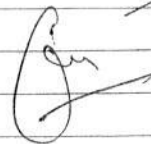(7) Precaution :- (i) Connection should be neat and clean.  
(ii) Connection should be tight.



  
Director  
Shri Pragya Mahavidyalaya  
Bilainagar-305624

Teacher's Signature : .....

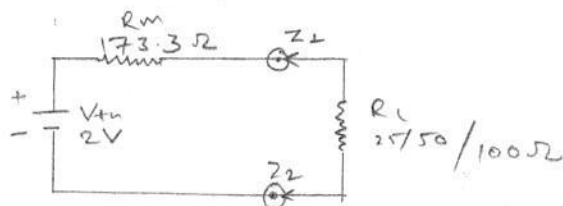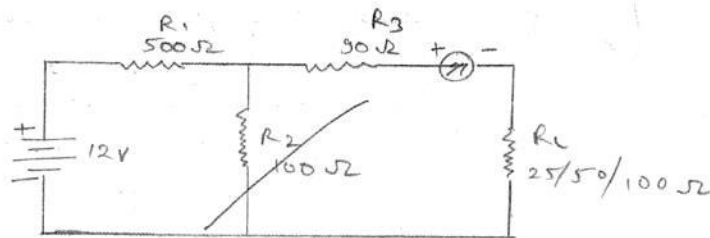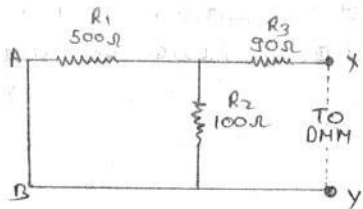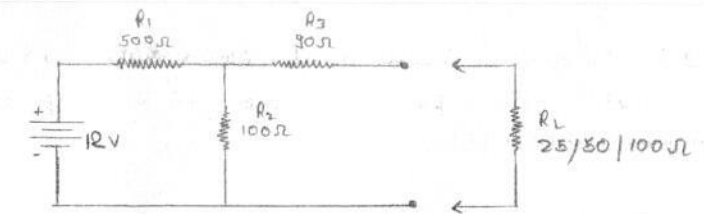

  
**Director**  
 Shri Pragya Mahavidyalaya  
 Bilainagar-305624

Experiment :- 2 Thevenin's Theorem

- (1) Object :- Verification of Thevenin's theorem.
- (2) Apparatus :- Box, ammeter, connecting wire, etc.
- (3) Theory :- It states that current flowing through a load resistance  $R_L$  connected across any two terminals of a linear active bilateral network is given by  $V_{oc} \parallel (R_{th} + R_L)$ , where  $V_{oc}$  is the open circuit voltage (i.e. voltage across the two terminals when  $R_L$  is removed) and  $R_{th}$  is the internal resistance of the network as viewed back into the open circuited network when all voltage sources are replaced by their internal resistances.
- (4) Observation :- Least count of ammeter =  $\frac{3}{10} = 0.3$

$V_{th} = 2V$  ;  $R_{th} = 173.3 \Omega$

(5) Observation Table :-

S.No	Load Resistance	Practical value	Calculated value
1.	25Ω	10 mA	9.5
2.	50Ω	8.9 mA	8.7
3.	100Ω	7.3 mA	7.2

Teacher's Signature : .....

(c) Calculation :- The value of resistance ( $R_{th}$ ) :-

$$R_{th} = [R_1 || R_2] + R_3 \Omega$$

$$R_{th} = \left[ \frac{500 \times 100}{500 + 100} \right] + 90 = 173.3 \Omega$$

$$V_{th} = 2V$$

for :-  $R_L = 25 \Omega$

$$I_L = \frac{V_{th}}{R_{th}} + R_L = \frac{2}{173.3} + 25 = 10 \text{ mA}$$

for :-  $R_L = 50 \Omega$

$$I_L = \frac{2}{173.3} + 50 = 8.9 \text{ mA}$$

for :-  $R_L = 100 \Omega$

$$I_L = \frac{2}{173.3} + 100 = 7.3 \text{ mA}$$

Date .....


Expt. No. ....

Page No. ... A .....

(7) Result :- The value of theoretical value and calculated value is approx. same hence, Thevenin theorem verified.





(8) Precaution :-  
(i) Wires should be connected neatly.  
(ii) Connection should be tight.

G

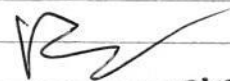

**Director**  
**Shri Pragma Mahavidyalaya**  
**Bilainagar-305624**

Teacher's Signature : .....

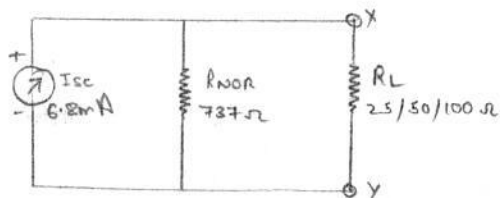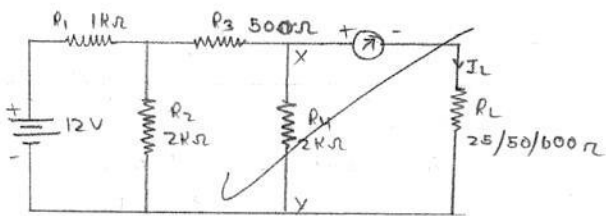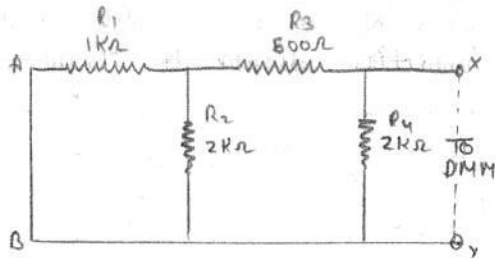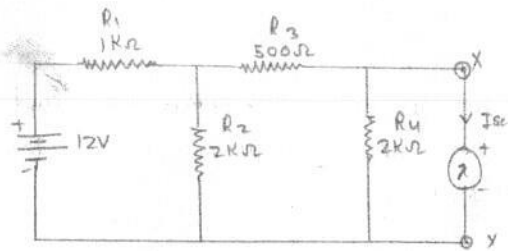

Experiment - 3 Norton Theorem

(1) Object :- Verification of Norton's Theorem.

(2) Apparatus :- Box, connecting wire, etc.

(3) Theory :- Norton theorem states that any two terminals active network containing voltage sources and resistance when viewed from its output terminal is equivalent to a constant current source ( $I_{sc}$ ) and a parallel resistance ( $R_{no}$ ). The constant current is equal to the current which would flow in a short circuit placed across the terminals and parallel resistance is the resistance of the network when viewed from these open circuited terminals after all voltage source have been removed and replaced by their internal resistance.

(4) Observation Table :-

S.No.	Load Resistance	Theoretical value	Calculated value
1.	25Ω	6.55 mA	6.60 mA
2.	50Ω	6.34 mA	6.35 mA
3.	100Ω	5.99 mA	6 mA

  
**Director**  
 Teacher's Signature  
**Shri Pragya Mahavidyalaya**  
 Bijainagar-305624

5) Calculation :- for resistance ( $R_{\text{NOR}}$ ) :-

$$R_{\text{NOR}} = [R_1 \parallel R_2 + R_3] \parallel R_4 \Omega$$

$$R_{\text{NOR}} = 737 \Omega$$

for short circuit current ( $I_{\text{sc}}$ ) :-

$I_{\text{sc}} = \frac{V_{\text{NOR}}}{R_{\text{NOR}}}$  → where  $V_{\text{NOR}}$  is open circuit voltage and is 5V

$$I_{\text{sc}} = \frac{5V}{737} = 6.78 \text{ mA}$$

for :-  $R_L = 25 \Omega$

$$I_L = \frac{6.78 \times 737}{737 + 25} = 6.55 \text{ mA}$$

for :-  $R_L = 50 \Omega$

$$I_L = \frac{6.78 \times 737}{737 + 50} = 6.34 \text{ mA}$$

for :-  $R_L = 100 \Omega$

$$I_L = \frac{6.78 \times 737}{737 + 100} = 5.94 \text{ mA}$$

Date .....

Expt. No. ....



Page No. 6

(6) Result :- Calculated value and observed value is approx. same hence Norton theorem is verified.

(7) Precaution :- (i) Connection should be neat and clean  
(ii) Connection should be tight.

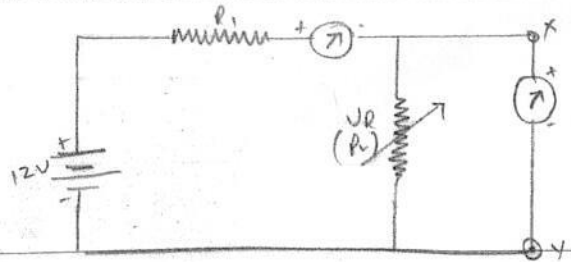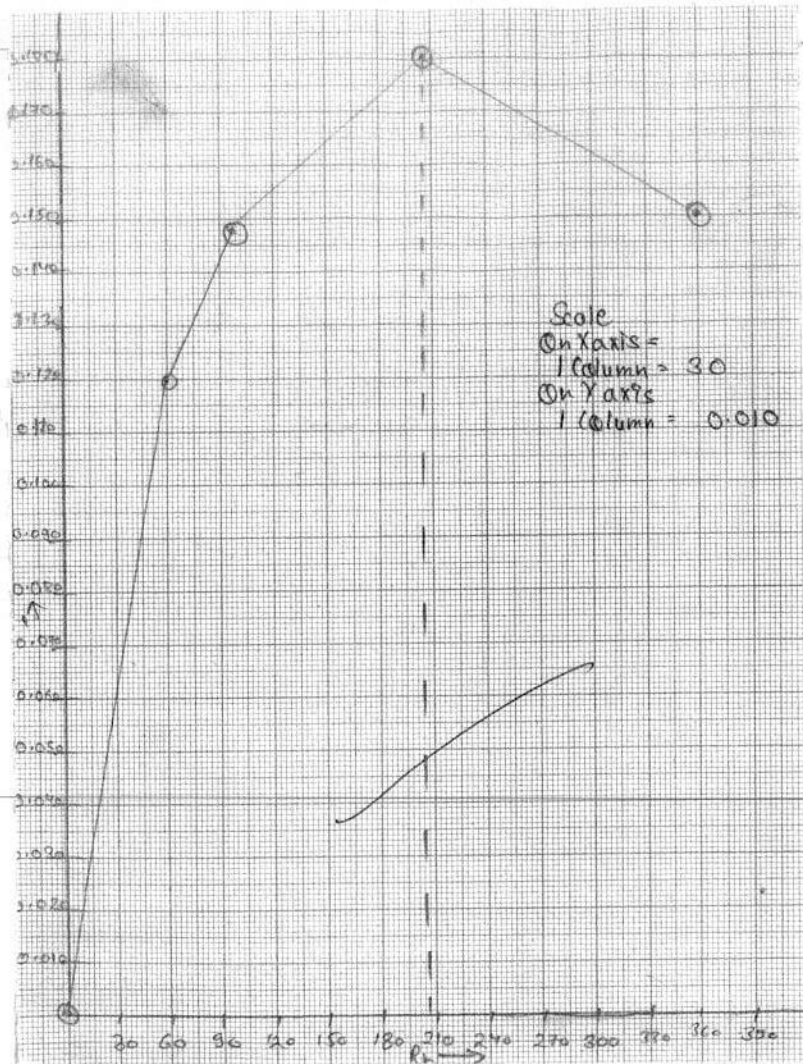(6)

  
Director  
Shri Pragma Mahavidyalaya  
Bilainagar-305624



Experiment - 4 Maximum Power Transfer Theorem

- (1) Object :- Verification of Maximum Power Transfer Theorem.
- (2) Apparatus :- Box, connecting wire, etc.
- (3) Theory :- When load is connected across a voltage source power is transferred from the source to the load. The amount of power transferred will depend upon the load resistance. If ' $R_L$ ' is made equal to the internal resistance ' $R$ ' of source then maximum power is transferred to the load ' $R_L$ '.

(iv) Observation Table :-

S.No	R	$P_L$ (W)	Voltage (V)	Current (I)	$P_{out} = VI$
1	200	0	0	0.06	0
2	200	48	2.4	0.05	0.12
3	200	97.5	3.9	0.04	0.156
4	200	200	6	0.03	0.18
5	200	330	7.8	0.02	0.15
6	200	400	9	0.01	0.09
7					
8					
9					

*[Handwritten Signature]*



Calculation :-

$$\text{For } R_L = R_L = \frac{V}{I}$$

1. If  $V = 0$  Then,  $R_L = 0$   
 $I = 0.06$

2. If  $V = 2.4$  Then,  $R_L = \frac{2.4}{0.05} = 48 \Omega$   
 $I = 0.05$

3. If  $V = 3.9$  Then  $R_L = \frac{3.9}{0.04} = 97.5 \Omega$   
 $I = 0.04$

4. If  $V = 6$  Then  $R_L = \frac{6}{0.03} = 200 \Omega$   
 $I = 0.03$

5. If  $V = 7.8$  Then  $R_L = \frac{7.8}{0.02} = 390 \Omega$   
 $I = 0.02$

6. If  $V = 9$  Then  $R_L = \frac{9}{0.01} = 900 \Omega$   
 $I = 0.01$

Date .....

Expt. No. ....

Page No. 8

Result :- If  $R_L = R_{eq}$  206  
Then power transfer in load is maximum.

Precaution :-


1. The load resistance  $R_L$  is varied from  $< R_s \text{ to } R_s >$
2. Internal resistance of the source should be measured before going to the experiment.
3. The battery should be removed and then terminal should while measuring the source resistance



  
Teach Director  
Shri Pragya Mahavidyalaya  
Bilaspur-305624

### Experiment-5 Anderson Bridge Method

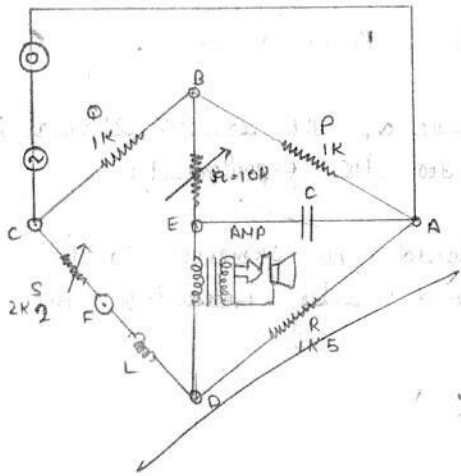- (1) Object :- To measure the inductance of a given coil by Anderson Bridge method.
- (2) Apparatus :- Small variable resistance, Galvanometer, audio oscillator, Battery, Plugs, Keys, Inductance Box, Connecting wire
- (3) Theory :- In Anderson bridge  $P$ ,  $Q$  and  $R$  are the non inductive variable resistance arms of the bridge & non inductive variable resistance 'S' in series with the given coil of unknown inductance 'L' is put in fourth arm of bridge between F and D. variable resistance 'S' and a variable condenser 'C' are put in parallel to resistance 'P'. An audio amplifier with speaker is put in between the point 'E' and 'D' and an audio frequency (fixed = 1000Hz) oscillator with a volume control is put between terminals of 'A' and 'C'.



For steady current and by equating real parts we have :-

$$L = \frac{C R (P S_1 + Q S_1 + P Q)}{P}$$

If  $P = Q$  then :-

$$L = C R (Q + 2 S_1)$$

where,

$L$  = unknown inductance ;  $C$  = condenser ;  $S_1$  = variable resistance

Teacher's Signature : .....

Formula :-  $L = CR(Q+2R)$

Calculations:-

For  $\mu = 2500$

$\rightarrow 0.0082 \times 1005 (1000 + 2 \times 2500) \times 10^{-6}$

$\rightarrow 0.0082 \times 1005 (6000) \times 10^{-6}$

$\rightarrow 49.4 \text{ mH}$

For  $\mu = 1900$

$\rightarrow 0.01 \times 1005 (1000 + 2 \times 1900) \times 10^{-6}$

$\rightarrow 0.01 \times 1005 \times 4800 \times 10^{-6}$

$\rightarrow 48.2 \text{ mH}$

For  $\mu = 800$

$\rightarrow 0.015 \times 1005 (1000 + 2 \times 800) \times 10^{-6}$

$\rightarrow 0.015 \times 1005 \times 2600 \times 10^{-6}$

$\rightarrow 39.195 \text{ mH}$

For  $\mu = 700$

$\rightarrow 0.022 \times 1005 (1000 + 2 \times 700) \times 10^{-6}$

$\rightarrow 0.022 \times 1005 \times 2400 \times 10^{-6}$

$\rightarrow 53.06 \text{ mH}$

For  $\mu = 600$

$\rightarrow 0.033 \times 1005 (1000 + 2 \times 600) \times 10^{-6}$

$\rightarrow 0.033 \times 1005 \times 2200 \times 10^{-6}$

$\rightarrow 72.96 \text{ mH}$

Expt. No. ....

P, Q, R = arm resistances

(u) Observation Table :-

S.No.	P ohm	Q ohm	R ohm	C	$\mu$ ohm	L	Mean L
1.	1000	1000	1005	0.082	2.5 x 1000	49.4 mH	
2.	1000	1000	1005	0.01	1.9 x 1000	48.2 mH	
3.	1000	1000	1005	0.015	0.8 x 1000	39.195 mH	52.563 mH
4.	1000	1000	1005	0.022	0.7 x 1000	53.06 mH	
5.	1000	1000	1005	0.033	0.6 x 1000	72.96 mH	


(5) Result :-  $L = 52.5 \text{ mH}$


So the self-inductance of given coil is  $52.5 \text{ mH}$

(A) Precautions:-


i) Avoid loose connection

ii) When under balanced condition occurs switch off the power supply - Take reading.

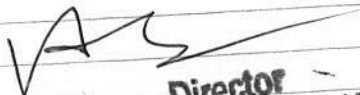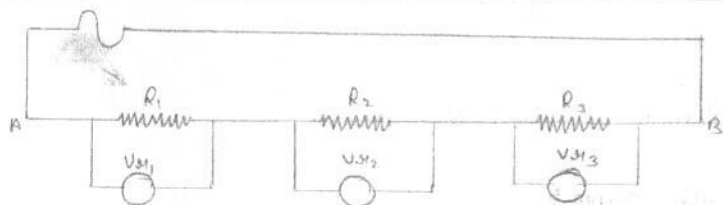
  
 Director  
 Teacher's Signature  
 Sri Pragya Mahavidyalaya  
 Mainagar-305624




Resistance in Series in AC circuit

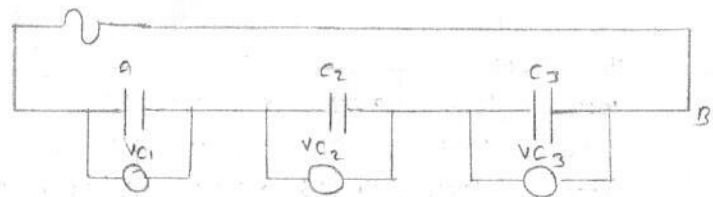

Condensers in Series in AC circuit

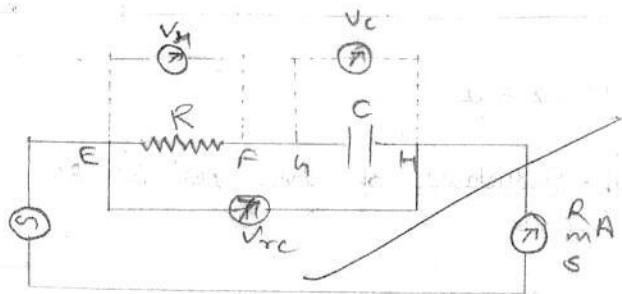

R-C circuit

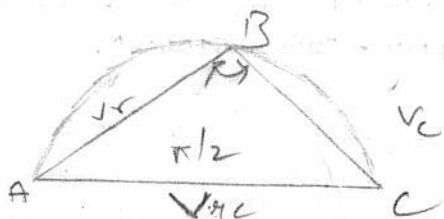

Phase difference b/w Vr & Vc

Experiment - 6

Object - To study R-C circuit using AC mains

Apparatus - R-C box, Connecting wire etc.

Principle - AC circuit will obey ohm's laws only if it has emitted R or C or L in series with it. If a combination of R & C or R & L or R & L & C is there, ohm's law is not obeyed.

If  $V_{r1}, V_{r2}, \dots$  &  $V_{c1}, V_{c2}$  etc are the voltage exp. across resistance & condenser then -

$$\frac{V_{r1}}{R_1} = \frac{V_{r2}}{R_2} = \frac{V_{r3}}{R_3} = i \text{ (constant)}$$

$$\frac{V_{c1}}{1/\omega C_1} = \frac{V_{c2}}{1/\omega C_2} = \frac{V_{c3}}{1/\omega C_3} = i$$

$$\omega C_1 V_{c1} = \omega C_2 V_{c2} = \omega C_3 V_{c3} = i \text{ (constant)}$$

Here,  $\omega$  is angular frequency =  $2\pi f$ ;  $f = 50 \text{ Hz}$ .

for A.C. mains here  $\frac{1}{\omega C}$  is resistance equivalent

to resistance.

*[Signature]*  
Teacher's Sign

Expt. No. ....

If 'V' is potential difference across A and B in two circuit then :-

$$V = V_{x1} + V_{x2} + V_{x3} \dots$$

$$\text{or, } V = V_{c1} + V_{c2} + V_{c3}$$

If R and C are connected in series then :-

$$V_{sc} < V_R + V_C$$

where,

$V_{sc}$  = potential difference across both R and C

As  $V_R$  and  $V_C$  are vector quantities :-

$$\vec{V}_{sc} = \vec{V}_R + \vec{V}_C$$

$$V_{sc}^2 = V_R^2 + V_C^2$$

Angle b/w  $V_R$  and  $V_C$  is  $\pi/2$  called phase difference

(4) Observation Table :-

Table-I

S.No	Resistor in series			Capacitor in series			
	R	$V_R$	$i = V_R/R$	C	$V_C$	$V_C / 1/\omega C$	$V_C V_C = i$
	5K	4.0	0.000812.3	1MAD	2.5	1.6	0.785mA
	10K	8.3	0.000832.3	0.47MAD	5.5	1.5	0.811mA
	15K	8.4	0.000842.2	0.22MAD	12.0	1.4	0.828mA

Teacher's Signature : .....

Director

Shri Pragna Mahavidyalaya  
Mangaluru-305624

Calculation :-

$$(1) i = \frac{4.0}{5 \times 1000} = 0.00081 \text{ Amp} = 0.81 \text{ mA}$$

$$(2) i = \frac{8.3}{10 \times 1000} = 0.00083 \text{ Amp} = 0.83 \text{ mA}$$

$$(3) i = \frac{8.4}{10 \times 1000} = 0.00084 \text{ Amp} = 0.84 \text{ mA}$$

$$\frac{V_{x1}}{R_1} = \frac{V_{x2}}{R_2} = \frac{V_{x3}}{R_3} = i \text{ (Constant)}$$

$$0.81 \text{ mA} \approx 0.83 \text{ mA} \approx 0.84 \text{ mA} \approx 0.82 \text{ mA}$$

$$\begin{aligned} (1) \omega \times C_1 \times V_{c1} \\ = 100 \pi \times 10 \times 10^{-6} \times 2.5 \\ = 7.85 \text{ mA} \end{aligned}$$

$$\begin{aligned} (2) \omega \times C_2 \times V_{c2} \\ = 100 \times 0.47 \times 10^{-6} \times 5.5 \\ = 0.81 \text{ mA} \end{aligned}$$

$$\begin{aligned} (3) \omega \times C_3 \times V_{c3} \\ = 100 \pi \times 0.22 \times 10^{-6} \times 12 \\ \approx 0.826 \text{ mA} \end{aligned}$$

$$\omega C_1 V_{c1} = \omega C_2 V_{c2} = \omega C_3 V_{c3} = I \text{ (Constant)}$$

$$0.785 \text{ mA} = 0.811 \text{ mA} = 0.826 \text{ mA} = 0.8 \text{ (Constant)}$$

$$V = V_{x1} + V_{x2} + V_{x3}$$

$$V = 4.0 + 8.3 + 8.4$$

$$V = 20.4$$

$$V = V_{c1} + V_{c2} + V_{c3}$$

$$V = 2.5 + 5.5 + 12.0$$

$$V = 20.2$$

Calculation for  $V_{RC}$

$$V_{RC} < V_{R1} + V_C$$

①  $20.1 < 19.5 + 5.7$   
 $20.1 < 25.2$

②  $20.4 < 16.4 + 12.0$   
 $20.4 < 28.4$

③  $20.5 < 20.3 + 2.5$   
 $20.5 < 22.8$

$$V_{RC}^2 = V_{R1}^2 + V_C^2 \quad (20.1)^2 < (19.5)^2 + (5.7)^2$$

①  $(20.1)^2 < (19.5)^2 + (5.7)^2$   
 $404.01 < 380.25 + 32.49$   
 $404.01 \approx 397.30$

②  $(20.4)^2 < (16.4)^2 + (12.0)^2$   
 $416.16 \approx 412.96$

③  $(20.5)^2 < (20.3)^2 + (2.5)^2$   
 $420.25 \approx 418.34$

*AS*  
**Director**  
 Pragya Mahavidyalaya  
 13gar-305624

Table-II

S.No	Voltage across R ( $V_{R1}$ )	Voltage across C ( $V_C$ )	$V_{R1} + V_C$	$V_{RC}$	$V_{R1}^2 + V_C^2$	Angle $\theta$ or $V_{RC}^2$
	19.5	5.7	25.2	20.1	397.30	/
	12.0	16.4	28.4	20.4	412.96	
	2.5	20.3	22.8	20.5	418.34	

Result's-

For resistance :-

$$\frac{V_{R1}}{R_1} = \frac{V_{R2}}{R_2} = \frac{V_{R3}}{R_3} = I \text{ (constant)}$$

For Condensers :-

$$wC_1 V_1 = wC_2 V_2 = wC_3 V_3 = I \text{ (constant)}$$

According to ohm law :-

$$V_{R1} + V_{R2} + V_{R3} = \text{input}$$

$$V_C + V_{R2} + V_{R3} = \text{input}$$

∴ Resistance R and Condenser C obey ohm's law

For R-C combination :-

$$V_{RC} < V_{R1} + V_C$$

$$(V_{RC})^2 = (V_{R1})^2 + (V_C)^2$$

Precaution :- ) The connection should be tight

) connection should neat & clean

Teacher's Signature : .....

Experiment :- 7

- 1) Object :- To measure the Impedance of R-C circuit.
- 2) Apparatus :- R-C circuit box, connecting wire etc.
- 3) Principle :- To measure the Impedance of R-C circuit  
formula required :-

$$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad \text{and} \quad Z = \frac{V_{RC}}{i}$$

where,  $R$  = Resistance

$C$  = Capacitance


$\omega$  = Angular frequency

$Z$  = Impedance

4) Observation Table :-

S.No	R	C	$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$	$V_{RC}$	$i$	$Z = \frac{V_{RC}}{i}$
	10K	1μF	10494.8749	19.8	4.1	$4.829269 \times 10^6$
	2K	0.47μF	7064.989	20.8	0.1	$208 \times 10^6$
	1K	0.22μF	14510.4687	1.2	2.5	$0.48 \times 10^6$

Teacher's Signature : .....

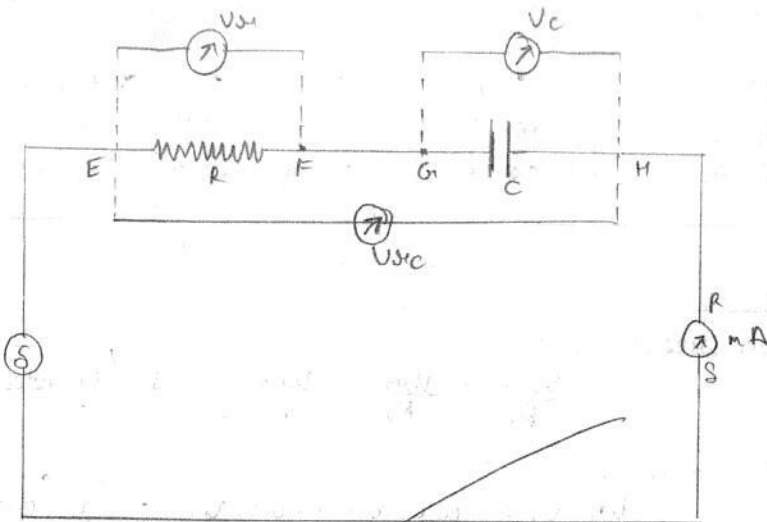Fig: R-C circuit

Director  
Shri Pragma Mahavidyalaya  
Bilainagar-305624

Calculation:-  $Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$

(i)  $R = 10000 \Omega$      $C = 1 \times 10^{-6} F$      $\omega = 100 \pi$

$$R = \sqrt{10000000 + \frac{1 \times 10^{12}}{10^4 \pi^2 \times 1}} = 10494.8749$$

(ii)  $R = 2000 \Omega$      $C = 0.47 \times 10^{-6} F$      $\omega = 100 \pi$

$$R = \sqrt{4000000 + \frac{1 \times 10^{12}}{10^4 \times \pi^2 \times (0.47)^2}} = 7064.9830$$

(iii)  $R = 1000 \Omega$      $C = 0.22 \times 10^{-6} F$      $\omega = 100 \pi$

$$R = \sqrt{1000000 + \frac{1 \times 10^{12}}{10^4 \pi^2 (0.22)^2}} = 14510.4687$$

Result:-

Theoretical value:- 10994.8749, 7064.9830, 14510.4687  
 Experimental value:  $4.829269 \times 10^6$ ,  $202 \times 10^6$ ,  $0.42 \times 10^6$

# Precaution:-

- (i) Range of millimeter should be suitably adjusted before taking readings.
- (ii) K means kilo ohm and  $\mu F$  means microfarad.

G

Director  
 Sri Pragna Mahavidyalaya  
 Bijnagar-305624  
 Teacher's Signature : \_\_\_\_\_



Experiment - 8 Spectrometer



Object :- To determine dispersive power of prism with the help of spectrometer.

Apparatus :- Spectrometer power of prism

Observation :-  $W = \frac{SV - SR}{SY}$

- ∴ SV = Angle of min. deviation for violet colour
- SR = Angle of min. deviation for red colour
- SY = Angle of min. deviation for yellow colour

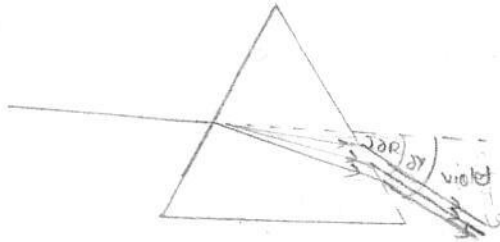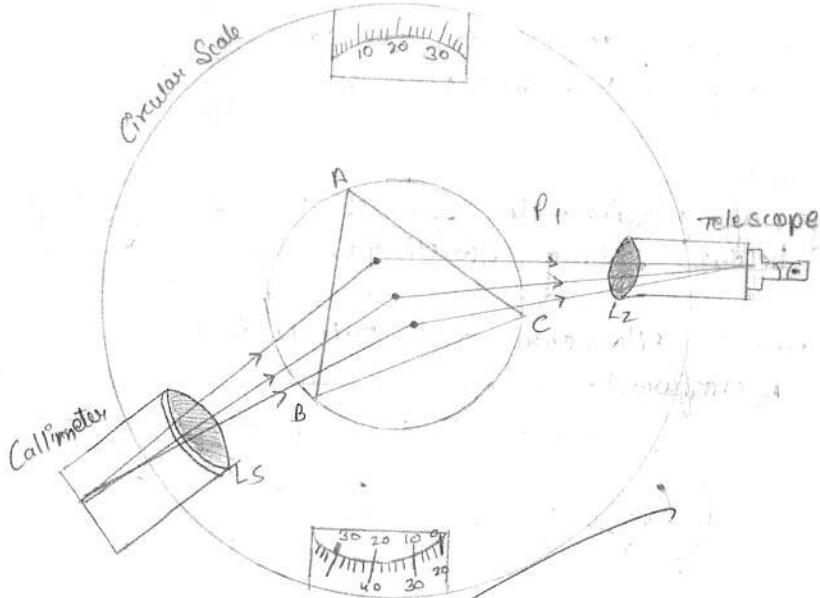One division of circular main scale of  $n = \frac{1}{3}$  degree  
 No. division on vernier (m) = 40 degree  
 Least count of vernier =  $\frac{\pi}{m} = \frac{1}{3 \times 40} = \frac{1}{120}$  degree



Director  
 Sri Pragya Mahavidyalaya  
 ...-305624

S.No	Colour	Minimum deviation Reading			Direct Reading			
		M.S	V.S	Total	M.S	V.S	Total	2a-b Mean
1.	Red	V <sub>1</sub>	$\frac{10}{60} = 0.16$	348.66	286.5	$\frac{20}{60} = 0.33$	286.83	61.83
		V <sub>2</sub>	$\frac{15}{60} = 0.25$	168.75	106.5	$\frac{15}{60} = 0.25$	106.75	62
2.	Yellow	V <sub>1</sub>	$\frac{1}{60} = 0.01$	348.51	286.5	$\frac{20}{60} = 0.33$	286.83	61.85
		V <sub>2</sub>	$\frac{18}{60} = 0.3$	168.8	106.5	$\frac{15}{60} = 0.25$	106.75	62.05
3.	Violet	V <sub>1</sub>	$\frac{3}{60} = 0.05$	345.55	286.5	$\frac{20}{60} = 0.33$	286.83	58.77
		V <sub>2</sub>	$\frac{9}{60} = 0.15$	165.65	106.5	$\frac{15}{60} = 0.25$	106.75	58.75

Teacher's Signature

Calculations:-

$$w = \frac{|S_1 - S_2|}{S_1}$$

$$= \frac{61.91 - 58.81}{61.86}$$

$$w = 0.05$$

Date .....


Expt. No. ....

Page No. 17

Result:- Dispersive power of prism  $w = 0.05$

Precaution:-

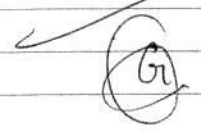The slit width must be very small but knife edges of the slit must not touch each other. do, as to get spectral



  
**Director**  
**Shri Pragma Mahavidyalaya**  
**Bilainagar-305624**

Teacher's Signature : .....

## Experiment - 9 Lee - Method

Object :- To determine the thermal conductivity of a solid non-metallic by Lee's Method.

Apparatus :- Disc, Hollow Cylinder, Insulator or Card board, Heating plate, Thermometer.

Theory :- The coefficient of Thermal Conductivity  $K$  is given by the formula

$$K = \frac{m \cdot s \cdot d}{(\theta_1 - \theta_2) \times \pi \cdot r_0} \times \frac{d\theta}{dt} \left[ \frac{2t + 2t}{2t + 2t} \right]$$

where,  $m$  = Mass of Disc plate over the experimental slab

$s$  = specific heat of material of Disc.

$d$  → Thickness of experimental Disc.

$r_0$  → radius of experimental Disc.

$\theta_1, \theta_2$  → Steady temperature of the two surface of experimental Disc.

$\left(\frac{d\theta}{dt}\right)$  → Rate of Reduction of two surface of the experimental Disc.


Observation :-

- i) Radius of Experimental Disc = 5.45 cm
- ii) Thickness 'd' of Experimental Disc = 1.21 cm
- iii) Mass of Brass Disc B = 918 gm
- iv) Specific heat 's' of Brass = 0.093 cal/gm

Teacher's Signature

Director

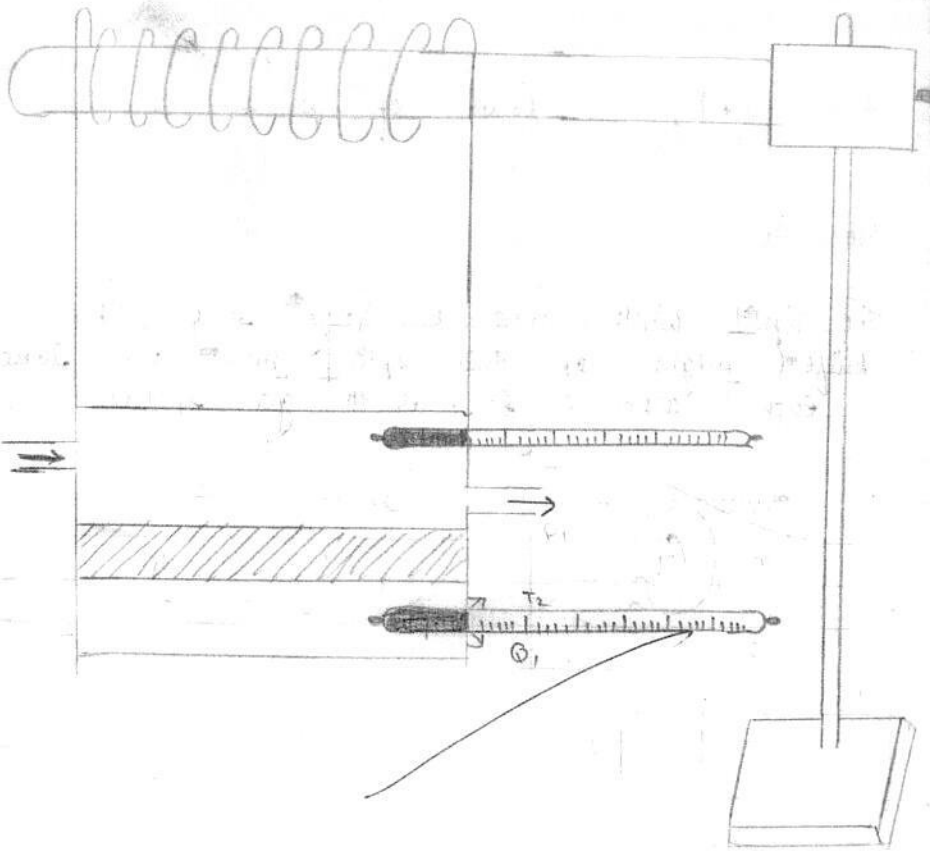Shri Pragna Mahavidyalaya  
Baramulla 305624



Calculation:-

$$K = \frac{msd}{(\theta_1 - \theta_2) \pi r^2} \times \frac{d\theta}{dt} \left( \frac{r_1 + 2r_2}{2r_1 + 2r_2} \right)$$

$$\theta_1 = 97^\circ\text{C}$$

$$\theta_2 = 78^\circ\text{C}$$

$$m = 918 \text{ gm}$$

$$s = 0.093 \text{ cal/gm}$$

$$d = 0.337 \text{ cm}$$

$$r_1 = 5.45 \text{ cm}$$

$$r_2 = 1.21 \text{ cm}$$

$$r_0 = 5.6 \text{ cm}$$

$$K = \frac{918 \times 0.093 \times 0.337}{(97 - 78) \times 3.14 \times (5.6)^2} \times \left( \frac{9.5}{6 \times 60} \right) \times \left( \frac{5.45 + 2 \times 1.21}{2 \times 5.45 + 2 \times 1.21} \right)$$

$$= \frac{28.771}{1870.93} \times \frac{9.5}{360} \times \frac{7.87}{13.82}$$

$$= \frac{2151.06}{8971483.53}$$

$$= 0.00023977 \text{ cal/gm}$$

Date

Expt. No.

Page No. 19

v) Radius of Insulator plate = 5.6 cm

vi) Thickness of Insulator plate = 0.337 cm

$$\theta_1 = 97$$

$$\theta_2 = 78$$

Observation Table:-

S.No.	Time	Temperature $\theta_1$ ( $^\circ\text{C}$ )	Temperature $\theta_2$ ( $^\circ\text{C}$ )
1.	5 minute	97	78
2.	10 minute	97	78
3.	15 minute	97	78
4.	20 minute	97	78
5.	25 minute	97	78


To obtain  $\frac{d\theta}{dt}$

S.No.	Time (minutes)	Temperature of Disc ( $^\circ\text{C}$ )
1.	0 minute	88 $^\circ\text{C}$
2.	1 minute	86 $^\circ\text{C}$
3.	2 minute	85 $^\circ\text{C}$
4.	3 minute	83 $^\circ\text{C}$
5.	4 minute	81 $^\circ\text{C}$
6.	5 minute	80
7.	6 minute	78.5
8.	7 minute	77
9.	8 minute	75.5
10.	9 minute	74
11.	10 minute	73

Teacher's Signature

Director

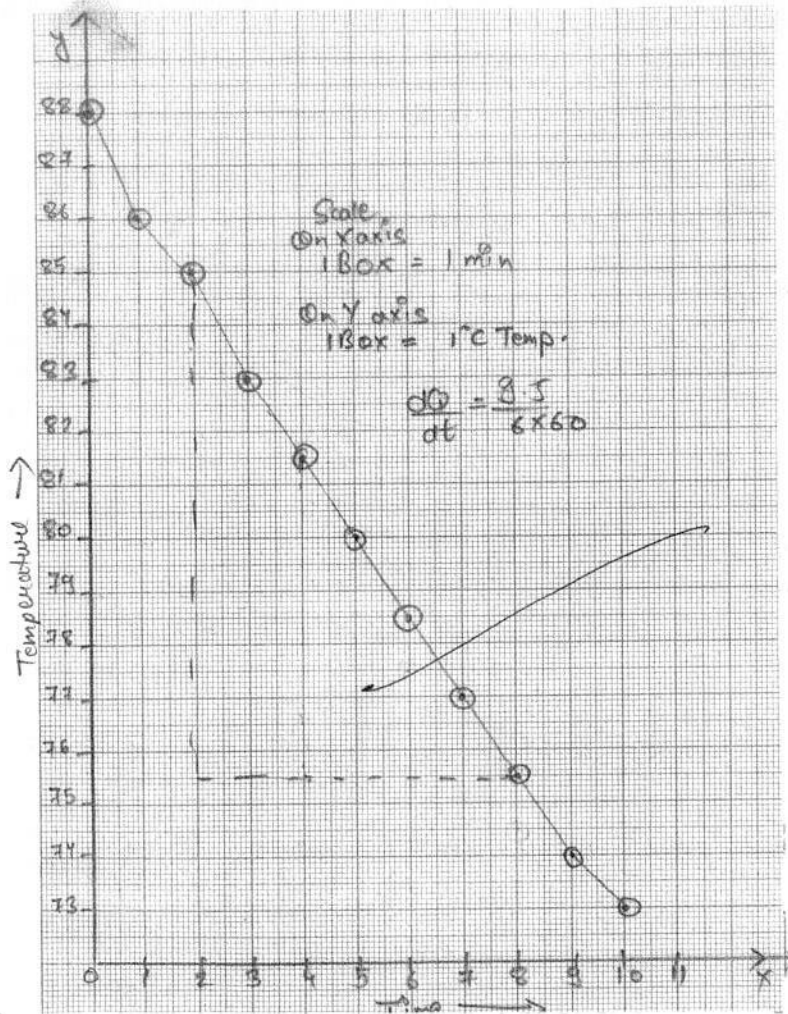Jhri Pragma Mahavidyalaya  
Bilainagar-305624



Result:- The coefficient of thermal conductivity of given sand board is  $0.0002397 \text{ cal/gmsec}$


Precaution :-

- i) observation for  $d$  and  $m$  of the experimental Disc should be taken before starting experimental accurately.
- ii) The steady state should be obtained very accurately
- iii) Experimental Disc should be thin.
- iv) The value of  $(\frac{dQ}{dt})$  from the graph should be obtained at  $\theta_2$  temperature ( $\theta_2$ )

(Signature)

(Signature)

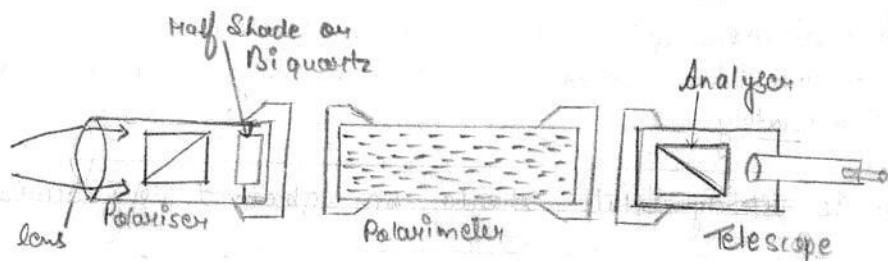**Director**  
Shri Pragma Mahavidyalaya  
Tadipatri-305624



(Polarisation of Light)

Experiment - 10 (Polarisation of Light)

Object:- To determine the specific rotation of Conc sugar solution with the help of polarisation meter.

Apparatus:- polarimeter, a balance, measuring cylinder, beaker and source of light.

Theory:- The specific rotation of the plane of polarisation of sugar dissolved in water can be determined by the following formula.

$$S = \frac{\theta}{L \times C} = \frac{\theta \times V}{L \times m} = \frac{100}{L \times C}$$

where,  $\theta$  → rotation produced in degree.

$L$  → length of the tube in decimeter.

$m$  → mass of sugar in gm, dissolve in water.

$v$  → volume of sugar solution.

Observation:-

i) Preparation of Sugar Solution:-

Mass of the watch glass = 5mm or 11.5 cm  
 watch glass + sugar = 100 gm

Teacher's Signature

Director

Mass of sugar taken  $m = 10 \text{ gm}$

Volume of the solution  $V = 100 \text{ cm}^3$

Concentration of the solution  $= \frac{m}{V} = \frac{10}{100} = 0.1 \text{ gm/cm}^3$

2) Mass of sugar in second solution  $m = \frac{10}{2} = 5 \text{ gm}$

Volume of second solution  $V = 100 \text{ cm}^3$

Concentration of the second solution  $C = \frac{m}{V} = \frac{5}{100} = 0.05 \text{ gm}$

3) Mass of sugar in third solution  $m = \frac{m_1}{4} = 2.5 \text{ gm}$

Volume of third solution (50 cm<sup>3</sup> second solution)

50 cm<sup>3</sup> distilled water

$V = 100 \text{ cm}^3$

Concentration of third solution  $\frac{m}{V} = \frac{2.5}{100} = 0.0025 \text{ gm}$

∴ To find value of radiation angle  $\theta$

value of one division of main scale  
 $n = 10$

Least Count of vernier  $= \frac{x}{n}$

$\frac{x}{n} = \frac{1}{10} = 0.1$

B. length of the polarimeter tube = 20 cm

Room temperature = 25°C

AS

Teacher's Signature

Director

Shri Pragya Mahavidyalaya  
Bijainagar-305624

## Specific Rotation

$$S = \frac{10\theta}{20}$$

$$S = \frac{10}{20} \times 138.33$$

$$S = 69.41 \text{ decimal/gm/cm}^3$$

Date .....

Expt. No. ....

Page No. 23

S.No	Liquid in Polarimeter tube	Status of Analyser						Mean Value	Rotating angle
		Anti Clock wise			Clock wise				
		M.S	V.S	Total	M.S	V.S	Total		
1	Distill. water	97	6x.1 = 6.6	97.6	275	7x.1 = 0.7	275.7	186.65	a =
2	10% of Sol <sup>n</sup>	110	7x.1 = 0.7	110.7	291	8x.1 = 0.9	291.9	201.3	b = b - a = 14.65
3	5% of Sol <sup>n</sup>	104.5	5x.1 = 0.5	105.0	282	9x.1 = 0.9	282.9	197.95	c = c - a = 7.3
4	2.5% of Sol <sup>n</sup>	101	8x.1 = 0.8	101.8	277	7x.1 = 0.7	277.7	189.75	d = d - a = 3.1

S.No	Concentration	rotation Angle (in degree)	$\frac{D}{C}$ (gm/cm <sup>3</sup> )	Mean D/C
1.	0.1	14.65	146.5	
2.	0.05	7.3	146	138.83
3.	0.025	3.1	124	


Result:- Specific rotation of sugar for light having temp. 25°C and wavelength 138.33 is 69.4 dec gm/cm<sup>3</sup> and percentage error is 4.5%  
Its authentic value = 66 decimal/gm/cm<sup>3</sup>

Precaution:- The polarimeter tube should be well cleaned.  
→ water used should be dust free.  
→ whenever a solution is changed rinse the tube with the new solution under examination.  
→ There should be no air bubble is left there.

*AW*

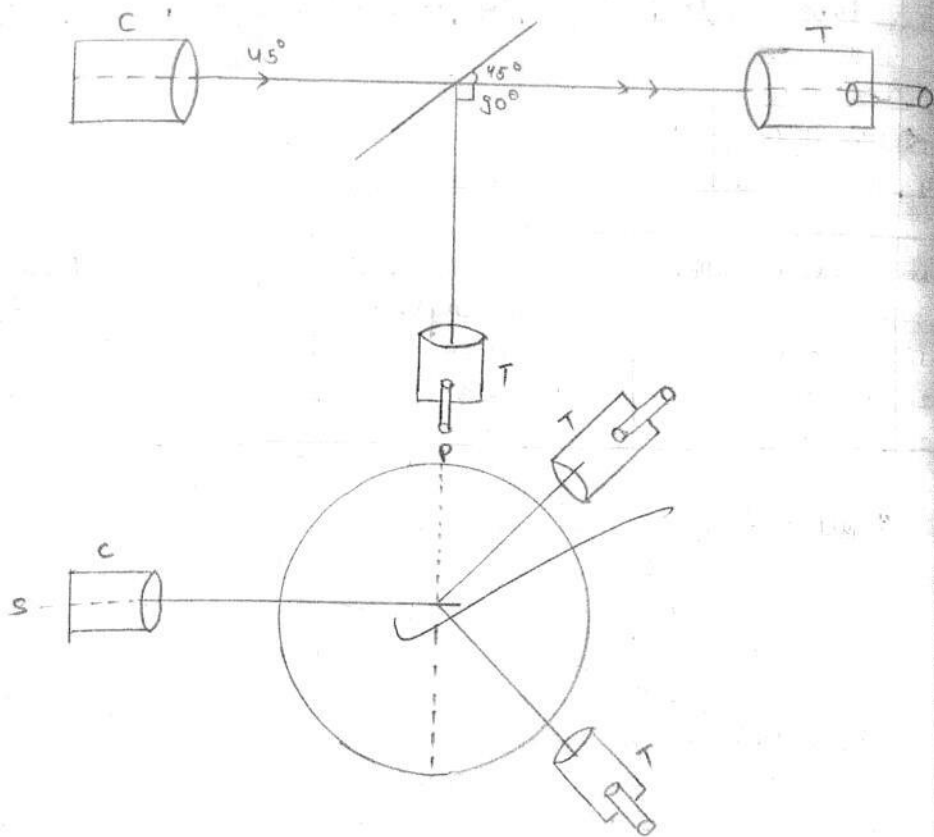Director  
Teacher's Signature  
Shri Pragma Mahavidyalaya  
Bijainagar-305624





### Experiment Diffraction of light

Object:- To determine the wavelength of prominent lines of mercury by plane diffraction grating

Apparatus:- A diffraction grating, spectrometer, mercury lamp, prism, reading lens.

Theory:- The wavelength  $\lambda$  of any spectral lines can be calculated by the formula

$$(a+b) \sin \theta = n\lambda$$

$$\lambda = \frac{(a+b) \sin \theta}{n}$$

where,  $(a+b)$  = grating element

$(\theta)$  = angle of diffraction

$(n)$  = order of the spectrum

Observation:-

(i) Finding the grating interval

No. of pattern grating lines = 15,000

$$\text{grating interval } (a+b) = \frac{2.54}{15000} = 1.69 \times 10^{-4} \text{ cm}$$

(ii) Finding the angle of diffraction

Teacher's Signature

Director

Calculation

(A) For Violet colour

$$\lambda_v = \frac{(e+b) \sin \theta}{n}$$

$$n = 1, (e+b) = \frac{2.54 \text{ cm}}{15000} = 1.69 \times 10^{-6} \text{ cm}$$

$$\theta_n = 12.5$$

$$\lambda_v = 1.69 \times 10^{-6} \times \sin(12.5) = 1.69 \times 10^{-6} \times 0.2164$$

$$= 0.3657 \times 10^{-6}$$

$$= 3657 \times 10^{-10}$$

(B) For Green colour

$$\lambda_g = \frac{(e+b) \sin \theta}{n}$$

$$\theta_n = 17 \quad \lambda_g = 1.69 \times 10^{-6} \times \sin(17) =$$

$$= 1.09 \times 10^{-6} \times 0.292$$

$$= 0.4941 \times 10^{-6}$$

$$= 4941 \times 10^{-10}$$

(C) For yellow colour

$$\lambda_y = \frac{(e+b) \sin \theta}{n}$$

$$\theta_n = 18 \quad \lambda_y = 1.69 \times 10^{-6} \times \sin(18) =$$

$$= 1.69 \times 10^{-6} \times 0.3090$$

$$= 0.3090 \times 1.69 \times 10^{-6}$$

$$= 0.52223 \times 10^{-6}$$

$$= 5222 \times 10^{-10}$$

$$\text{least count of scale (x)} = \frac{1}{24}$$

$$\text{Number of parts in vernier (N)} = 30$$

$$\text{Vernier least count} = \frac{x}{n} = \frac{1}{24 \times 30} = \frac{1}{60}$$

$$\text{Apparent order} = \frac{\theta}{n} = \frac{1}{60}$$

$$n = (1)$$

Observation Table

S.No.	Colour	Spectrometry Reading							2θ = (a-b)	Mean
		Left side			Right side					
		Reading of telescope			Reading of telescope					
		M.S	V.S	Total	M.S	V.S	Total			
1	Violet	v <sub>1</sub>	328	1/60	328.01	303	1/60	303.01	25	12.5
		v <sub>2</sub>	148	1/60	148.01	123	1/60	123.01	25	12.5
2	Green	v <sub>1</sub>	332	1/60	332.01	298	1/60	298.01	34	17
		v <sub>2</sub>	152	1/60	152.01	118	1/60	118.01	34	17
3	Yellow	v <sub>1</sub>	333	1/60	333.01	297	1/60	297.01	36	18
		v <sub>2</sub>	153	1/60	153.01	117	1/60	117.01	36	18

Result :- For mercury light source

$$\lambda_v = 3657 \text{ \AA}$$

$$\lambda_g = 4941 \text{ \AA}$$

$$\lambda_y = 5222 \text{ \AA}$$

Standard value

$$\lambda_v = 4358 \text{ \AA}$$

$$\lambda_g = 5460 \text{ \AA}$$

$$\lambda_y = 5790 \text{ \AA}$$

Teacher Signature

Director

Expt. No. ....

Precaution :-

1. Before performing the exp. the spectrometer should be adjusted.
2. grating should be set normal to the incident light
3. grating should not be touched by fingers.
4. while taking observation telescope and prism table should be kept fixed.

  
Director  
Shri Pragma Mahavidyalaya  
Bilainagar-305624

## Experiment - 12 Random Decay

Object :- Study random decay using dices and to calculate logarithmic decrement, half life and mean life.

Apparatus :- Dice, Board, Box

Theory :- (i) It is not possible to predict when any given radioactive nuclei will decay but it is possible to predict the average rate of decay for a large number of nuclei within a given sample.

(ii) The decay of a radioactive substance is a random event. It is a statistical process.

(iii) We can use dices to simulate a specific number when tossed to study radioactive decay.

(iv) We can thus calculate by graph.

$$\text{Logarithm } (\lambda) = 2.303 \left( \frac{N_B}{N_C} \right)$$

Decrement

$$\text{Half life} = (T_{1/2}) = \frac{0.693}{\lambda}$$

$$\text{Mean life} = (T_m) = \frac{1}{\lambda}$$

  
Director  
Shri Pragya Mahavidyalaya  
Bilainagar-305624

Calculation:-

$$\lambda = 2.3026 \times \frac{PQ}{QR}$$

$$PQ = 2.75 - 2.43 = 0.32$$

$$QR = 7 - 3 = 4$$

$$\lambda = 2.3026 \times \frac{.32}{4}$$

$$\lambda = 0.1842$$

$$T_{1/2} = \frac{.693}{\lambda}$$

$$= \frac{0.693}{0.184}$$

$$= 3.76$$

Date .....

Expt. No. ....

Page No. 28

Observation:- Total no. of cube No = 100

Order of trial	No. of cube										No. of decayed Particle	No. of Undecayed Particle	log <sub>10</sub>
	I	II	III	IV	V	VI	VII	VIII	IX	X			
1.	15	14	26	16	21	16	16	21	17	12	174	826	2.91
2.	15	16	14	16	12	13	19	11	15	18	149	677	2.83
3.	9	11	12	10	8	11	7	15	9	13	105	572	2.75
4.	13	10	8	10	7	13	10	10	10	9	100	472	2.67
5.	10	9	5	7	8	9	10	5	7	6	76	386	2.59
6.	5	6	8	6	7	6	7	7	5	10	67	329	2.51
7.	5	11	3	5	7	3	3	9	5	4	55	274	2.43
8.	3	8	5	3	4	5	4	4	3	4	43	231	2.36
9.	3	4	1	4	4	2	5	3	4	2	32	199	2.29
10.	4	2	3	3	4	2	2	4	3	2	29	170	2.23

Model Calculation:-

$$\text{If } PQ = .32 \quad QR = 4$$


$$\lambda = 2.3026 \frac{PQ}{QR} = 2.3026 \times \frac{.32}{4}$$

$$= 2.3026 \times .08$$

$$= 0.1842$$

Director  
Teacher's Signature  
Shri Pragya Mahavidyalaya  
Bhainagar-305624

Graph b/w  $N$  and  $t$  :-

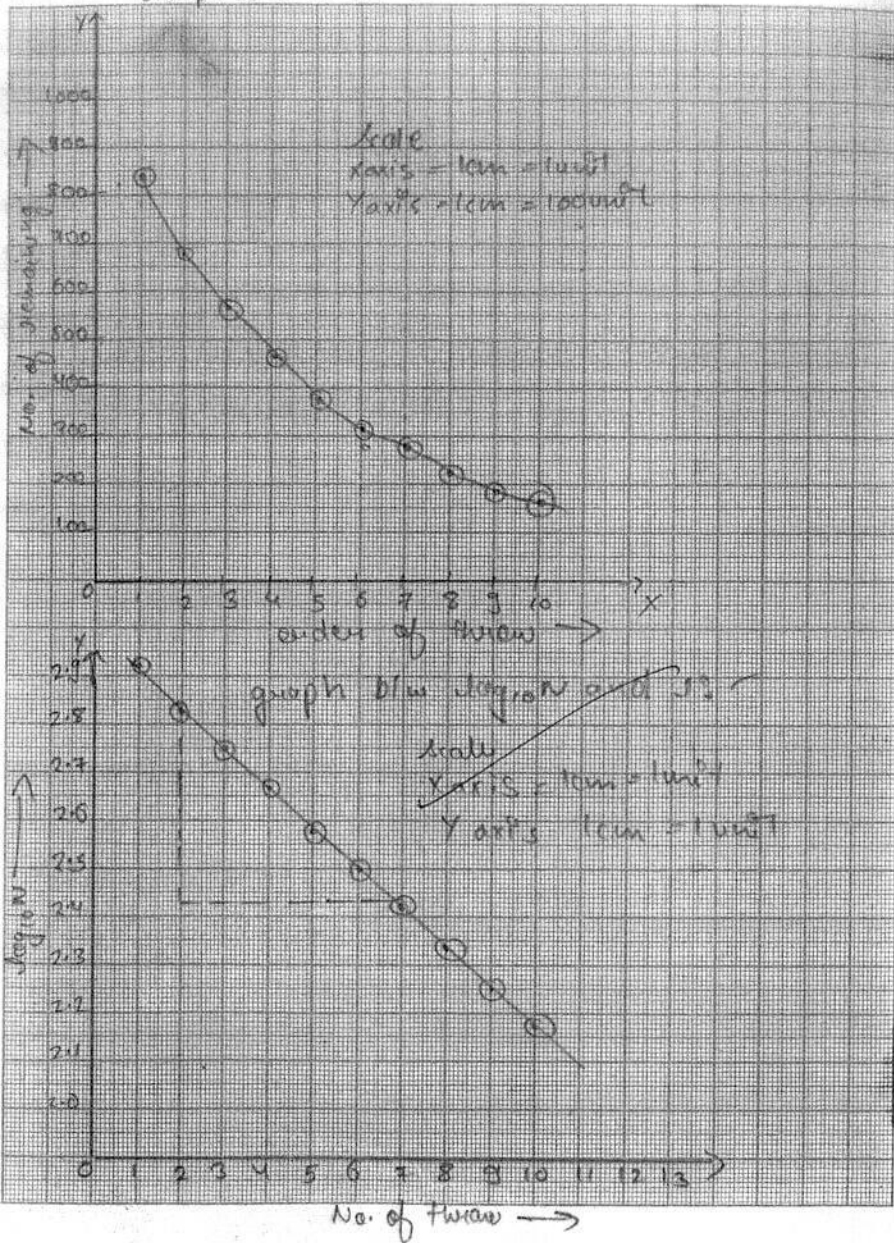

Expt. No. ....

Result :- 1) The graph drawn b/w  $N$  and  $t$  comes out to be an exponential decay curve.

2) The graph drawn b/w  $\log_{10} N$  and  $t$  comes out to be a straight line.

3) Decay constant  $\lambda = 0.1842$ ,  $T_{1/2} = 3.76$

4) Standard value  $\lambda = \frac{1}{6} = 0.1667$

$T_{1/2} = 4.2$

Precaution :-

- i) The no. of cubes must be large
- ii) All cubes are identical
- iii) Higher the repetition, lower the error
- iv) The cubes must be stirred well.

G

Director  
 Sri Pragya Mahavidyalaya  
 Mainagar-305624

Teacher's Signature .....